

Smart Garage System

BIRLA INSTITUTE OF TECHNOLOGY AND
SCIENCE,

PILANI

PILANI CAMPUS

PROJECT NUMBER: 21

GROUP NUMBER: 10

Yash Bansal : 2014B2A7238P


Aman Gupta : 2014B2A7358P

Abhishek Jain : 2014B2A7363P

Subham Swastik Dora : 2014B2A7644P

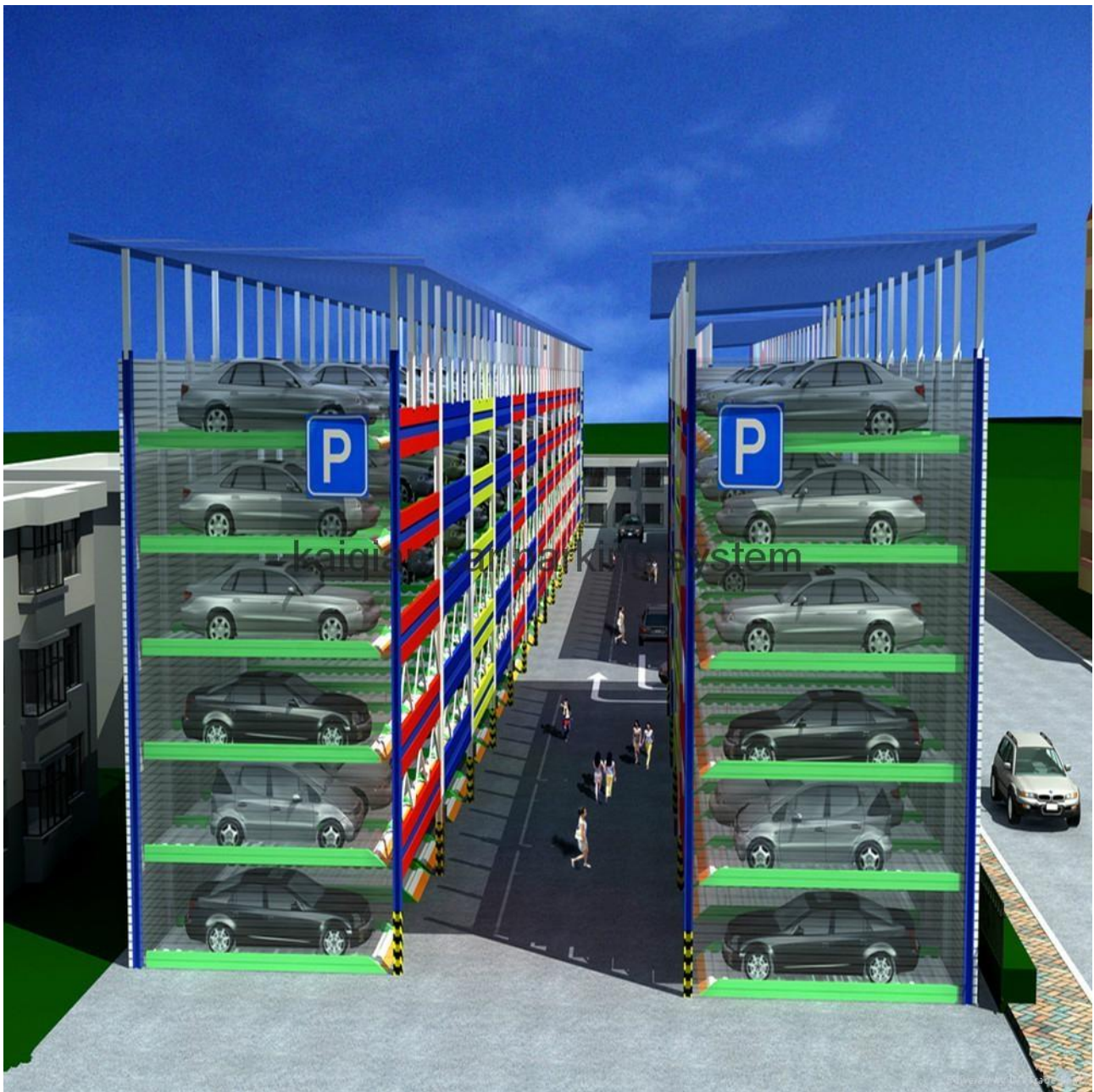Problem Statement:

To design a Smart Garage System to be used in an underground parking of a hotel with a maximum capacity of 2000 cars. A remote unit for opening and closing of the garage door would be with every user of the garage. The remote unit has only one button. A LCD display would be available indicating the number of cars in the garage. System runs from a standard power inlet available in the garage. Full and empty status will be shown through an LED.



Specifications:

- Remote unit button toggles the condition of the garage door- i.e. if the door is opened it is closed and vice versa.
- The remote unit is used for short distances only.
- A DC motor is used for opening and closing the door .The motor is a 50V ,3 A motor.
- The system distinguishes between a person and a car using a switch that can be closed only by the weight of a car.
- System is used in the hotel- so you can assume that a valet parking system is followed
this indicates that only one person leaves the garage after the car is parked and only a single person enters the garage to retrieve the car
- The system also has to distinguish between entry and exit by using two IR sensors on either side of the gate. Depending on the sequence in which the sensors are triggered (by man\car) , an entry or exit is recorded and the count of vehicles is changed accordingly in case of cars.
- Whether a car enters or a valet enters the door remains open for a period of five minutes. During these 5 minutes the system keeps checking if the remote is triggered.
- The door can close after 5 Minutes or when the valet uses the remote.
The remote can be used inside as well as outside the garage.
- An LCD screen (LM016L) is used to display the count of cars in the garage while an LED screen displays “FULL” when there are 2000 cars and “EMPTY” when there are no cars.

Components Used

Microprocessor	INTEL 8086	1
4 KB ROM chips	2732	4
2 KB RAM chips	6116	2
PPI	8255	2
TIMER	8253	2
LCD display	LCDLM016L	1
LED Display		2
3to 8 line Decoder	74LS138	2
AND gates	7408	1
OR gate		6
NOT gate	7404(six)	2
Motor Driver	LS239D	1
Motor	50 V , 3A	1
Bidirectional buffer	74LS245	2
Unidirectional buffers	74LS244	2
Unidirectional latches	74LS373	3

Clock Generator	8284	1
Comparator IC	LM139	1
IR receiver	TSOP 1738	3
Weight Sensor		1

ALGORITHM:

-To determine if a car/person is entering or leaving IR sensors are placed on both the inside and outside of the garage.

-The heavier car is differentiated from a person by using pressure transducers.

-A remote is also used for opening and closing of the garage. The sensors and remote signals are continuously checked for any valid input. A user can press the remote to open or close the garage.

-A count is kept for the number of cars in the garage which is updated whenever a car enters or leaves the garage. This count is displayed on the LCD screen and if the count is 2000, a red LED glows whereas in the case of 0, a green LED glows.

-Whenever a door is opened using a remote, it can be closed by pressing the remote again. Otherwise, it will automatically close after 5 minutes.

-When a car wants to enter the garage, then the user presses the remote. This would open the gate using the motor and the car can enter the garage. The door will remain open till the remote is again pressed else it will automatically close in 5 minutes. The count of cars will be updated.

-Whenever the valet wants to enter or leave the garage, the remote has to be pressed.

-When the car wants to leave the garage, the remote is pressed by the user. This would close the gate using the motor and the car can leave the garage. The door will remain open till the remote is again pressed else it will automatically close in 5 minutes. The count of cars is updated.

Assumptions:

-The garage is initially empty and the garage door is closed.

-Voltage reference for weight(force) sensor is 0.5V

-Voltage reference for IR sensors is 0.2V.

-The LED shows GREEN when the garage is empty, and shows RED when it is full, otherwise both wont light up.

-The remote is enabled manually by us on Proteus using buttons.

Memory Mapping:

Memory Interfacing Devices

ROM1_Even -> 00000h-01FFEh
ROM1_Odd -> 00001h-01FFFh
RAM1_Even -> 02000h-02FFEh
RAM2_Odd -> 02001h-02FFFh
ROM2_Even -> FE000h-FFFFEh
ROM2_Odd -> FE000h-FFFFFh

8255

PORT A -> 00h
PORT B -> 02h
PORT C -> 04h
CONTROL REGISTER -> 06h

Timer

COUNTER1 -> 08h
COUNTER2 -> 0Ah
COUNTER3 -> 0Ch
CONTROL REGISTER -> 0eh


Timer 2


COUNTER 1 -> 10h
COUNTER 2 -> 12h
COUNTER 3 -> 14h
CONTROL REGISTER->16h


Assignment of Input Ports


PA0->Remote Input
PA1->Outer_IR Input
PA2->Transducer(Weight Sensor)
PA3->Inner_IR Input
PA4->Remote Timer

Flow Chart:

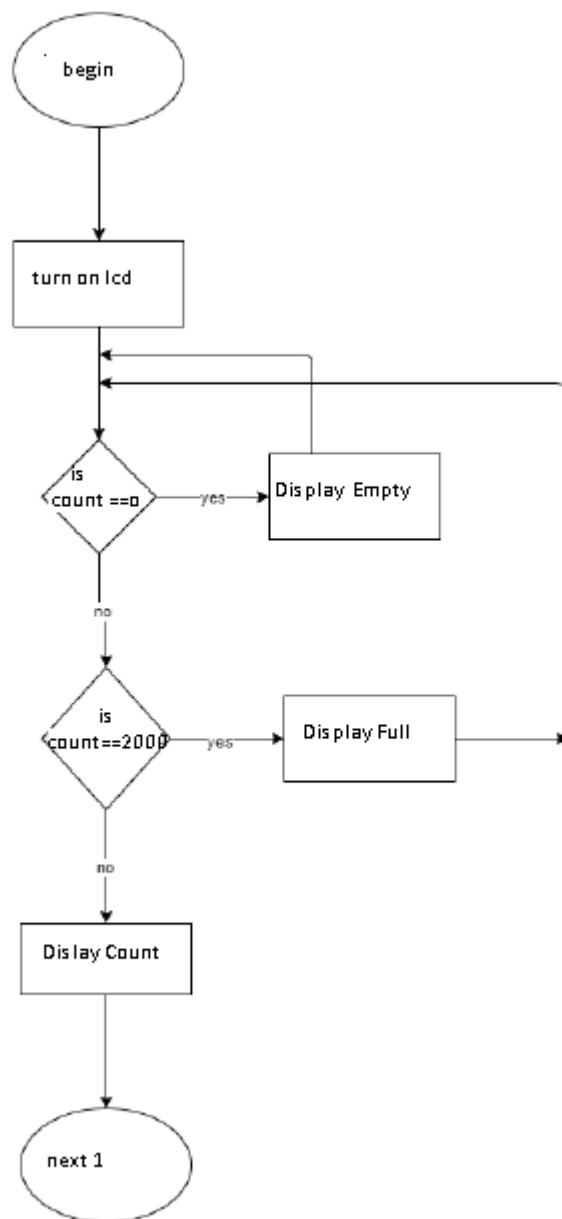

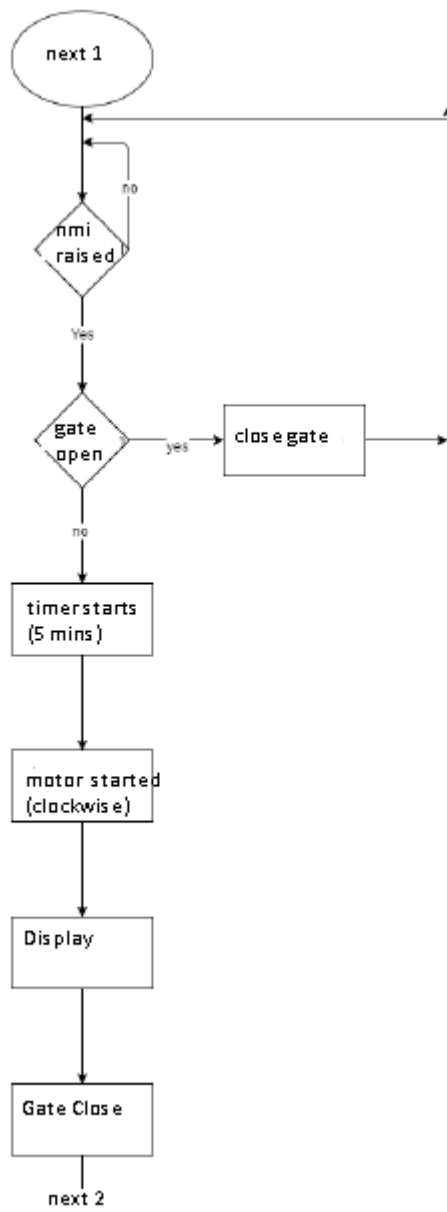

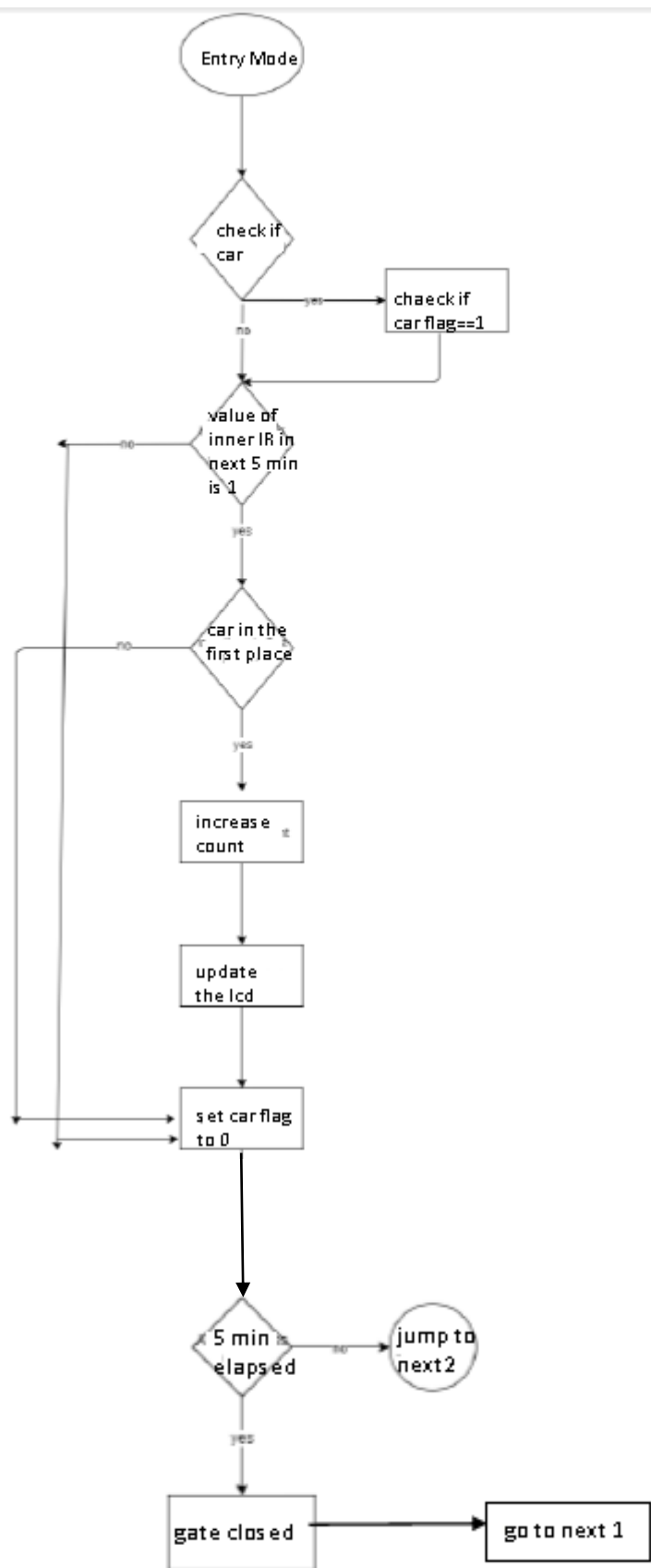

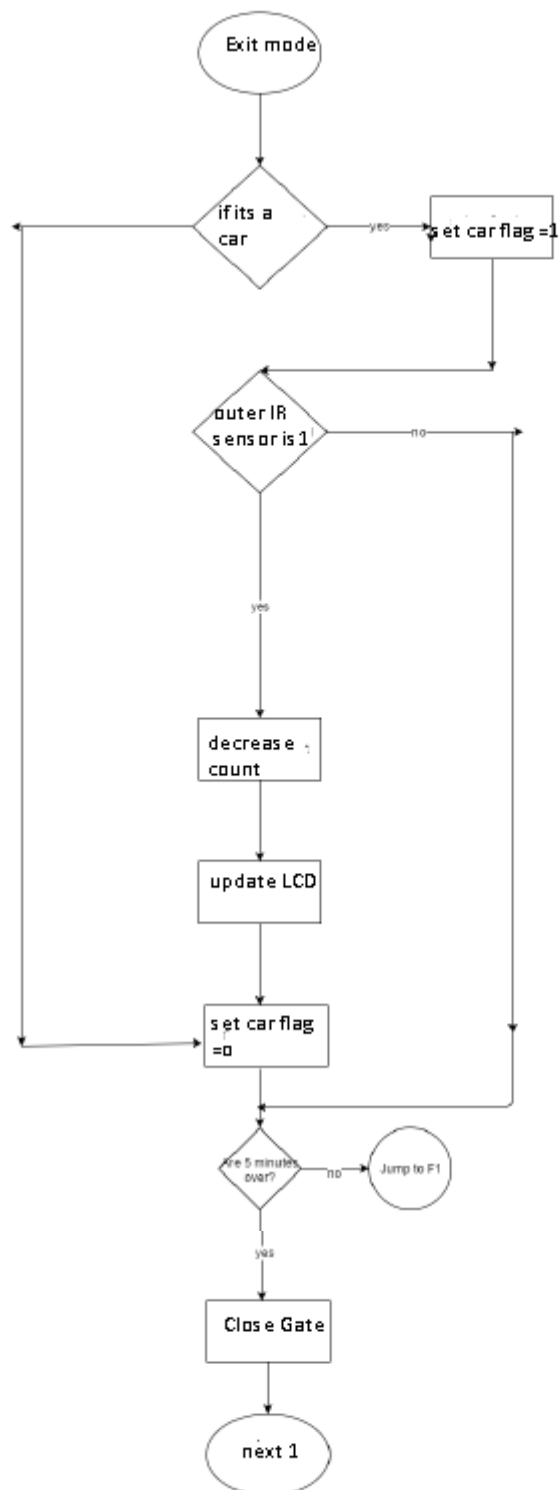

ASM CODE :

```

.model tiny
.8086

```

.data

```
strlen db 0
empty db 'EMPTY'
full db 'FULL'
count dw 0
```

;assigning port addresses

```
inadd_word equ 00h
lcd_data equ 02h
lcd_motor_control equ 04h
creg_io equ 06h
```

```
timer_clock equ 08h
timer_remote equ 0ah
timer_door equ 0ch
creg_timer equ 0eh
```

```
timer_clock2 equ 10h
timer_remote2 equ 12h
timer_door2 equ 14h
creg_timer2 equ 16h
```

```
jmp st1
db 1024 dup(0)
```

.code

.startup

st1:

```
mov cx, 0000h
mov bx, 0000h
mov dx, 0000h
```

inits:

```
mov ax,0200h
mov ds,ax
mov es,ax
mov ss,ax
mov sp,0FFFEH

mov al,10000000b
```

```
out creg_io,al
```

```
mov al, 00110110b  
out creg_timer, al  
mov al, 0A8h ;10101000  
out timer_clock, al ;Timer 1 intialize  
mov al, 61h ;01100001  
out timer_clock, al
```

```
mov al,00110011b ;Timer 2 intialize  
out creg_timer2,al
```

```
call lcd_init  
call lcd_update
```

garageclosed:

```
in al, inadd_word  
and al, 00000001b  
cmp al, 1  
je opendoor  
jmp garageclosed
```

garageopen:

```
mov cl,0  
mov ah, 0 ; reset car flag to 0  
in al, inadd_word  
mov bl, al  
and bl, 00000001b  
cmp bl, 00000001b ; check for remote press  
je closedoor  
mov bl, al  
and bl, 00010000b  
cmp bl, 00010000b ; check for timeout (5 minutes)  
je closedoor  
mov bl, al  
and bl, 00000010b  
cmp bl, 00000010b ; check for outer IR  
je entering  
mov bl, al  
and bl, 00001000b  
cmp bl, 00001000b ; check for inner IR  
je exiting  
jmp garageopen
```

closedoor:

```
call motor_clockwise
call motor_start
call start_door_timer
```

stillclosing:

```
    in al, inadd_word
    and al, 00100000b
    cmp al, 00100000b    ; wait for door to close completely
    jne stillclosing
```

```
call motor_stop
jmp garageclosed
```

opendoor:

```
call start_remote_timer
call motor_anticlockwise
call motor_start
call start_door_timer
```

stillopening:

```
    in al, inadd_word
    and al, 00100000b
    cmp al, 00100000b    ; wait for door to open completely
    jne stillopening
```

```
call motor_stop
jmp garageopen
```

entering:

```
mov cl,0
in al, inadd_word
mov bl, al
and bl, 00000001b
cmp bl, 00000001b
je closedoor
mov bl,al
and bl, 00010000b
cmp bl, 00010000b    ; check for timeout (5 minutes)
je closedoor
mov bl, al
and bl, 00000100b
cmp bl, 00000100b    ; check for car
jne nc00
mov ah, 1
```

nc00:

```
    mov bl, al
```

```

    and bl, 00001000b
    cmp bl, 00001000b    ; check for inner IR
    jne entering
    cmp ah, 1
    jne nc01
    inc count
    call lcd_update
nc01:
    in al, inadd_word
    mov bl, al
    and bl, 00001000b
    cmp bl, 00001000b    ; debounce
    je nc01
    jmp garageopen

```

exiting:

```

    mov cl,0
    in al, inadd_word
    mov bl, al
    mov bl, al
    and bl, 00000001b
    cmp bl, 00000001b
    je closedoor

    and bl, 00010000b
    cmp bl, 00010000b    ; check for timeout (5 minutes)
    je closedoor

    mov bl, al
    and bl, 00000100b
    cmp bl, 00000100b    ; check for car
    jne nc10

    mov ah, 1
nc10:
    mov bl, al
    and bl, 00000010b
    cmp bl, 00000010b    ; check for outer IR
    jne exiting
    cmp ah, 1
    jne nc11
    dec count

    call lcd_update
nc11:

```

```

    in al, inadd_word
    mov bl, al
    and bl, 00000010b
    cmp bl, 00000010b    ; debounce
    je nc11
    jmp garageopen

```

```

lcd_init proc near
    mov al, 00001111b
    out lcd_data, al
    mov bl, 00100000b
    call setlcdmode
    mov bl, 00000000b
    call setlcdmode
    ret
lcd_init endp

```

```

lcd_update proc near
    call lcd_clear
    mov al, ' '
    call lcd_add_lcd
    cmp count, 0
    jnz notempty
    lea di, empty
    mov strlen, 5
    jmp loaded
notempty:
    cmp count, 2000
    jnz notfull
    lea di, full
    mov strlen, 4
    jmp loaded
notfull:
    call lcd_bcd
    ret
loaded:
    call lcd_add_word
    ret
lcd_update endp

```

```

    lcd_bcd proc near
    mov ax, count
    mov cx, 0

```

converting:

```
    mov bl, 10
    div bl
    add ah, '0'
    mov bl, ah
    mov bh, 0
    push bx
    inc cx
    mov ah, 0
    cmp ax, 0
    jne converting
```

printing:

```
    pop ax
    call lcd_add_lcd
    loop printing
    ret
lcd_bcd endp
```

```
lcd_add_word proc near
    mov cl, strlen
```

putting:

```
    mov al, [di]
    call lcd_add_lcd
    inc di
    loop putting
    ret
lcd_add_word endp
```

```
lcd_add_lcd proc near
    push ax
    out lcd_data, al
    mov bl, 10100000b
    call setlcdmode
    mov bl, 10000000b
    call setlcdmode
    pop ax
    ret
lcd_add_lcd endp
```

```
lcd_clear proc near
    mov al, 00000001b
    out lcd_data, al
    mov bl, 00100000b
```

```
    call setlcdmode
    mov bl,00000000b
    call setlcdmode
    ret
lcd_clear endp
```

```
setlcdmode proc near
    in al, lcd_motor_control
    and al, 00011111b
    or al, bl
    out lcd_motor_control, al
    ret
setlcdmode endp
```

```
start_door_timer proc near
    mov al, 10110000b
    out creg_timer, al
    mov al, 90h
    out timer_door, al
    mov al, 01h
    out timer_door, al
    ret
start_door_timer endp
```

```
start_remote_timer proc near
    mov al, 01110000b
    out creg_timer, al
    mov al, 30h
    out timer_remote, al
    mov al, 75h
    out timer_remote, al
    ret
start_remote_timer endp
```

```
motor_stop proc near
    in al, lcd_motor_control
    and al, 11111100b
    or al, 00000000b
    out lcd_motor_control, al
    ret
motor_stop endp
```

```
motor_anticlockwise proc near
    in al, lcd_motor_control
```



```
    and al, 11111100b
    or al, 00000001b
    out lcd_motor_control, al
    ret
motor_anticlockwise endp
```

```
motor_clockwise proc near
    in al, lcd_motor_control
    and al, 11111100b
    or al, 00000010b
    out lcd_motor_control, al
    ret
motor_clockwise endp
```

```
motor_start proc near
    in al, 0cah
    out timer_clock2, al
    in al, 08h
    out timer_clock2, al
    in al, 0d4h
    out timer_clock2, al
    in al, 30h
    out timer_clock2, al
    ret
motor_start endp
```

```
.exit
end
```

