

CSE2006

Microprocessor & Interfacing

Module – 5

Introduction to Peripheral Interfacing II

Dr. E. Konguvel

Assistant Professor (Sr. Gr. 1),
Dept. of Embedded Technology,
School of Electronics Engineering (SENSE),
konguvel.e@vit.ac.in
9597812810



VIT[®]
Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

Module 5: Introduction Peripheral Interfacing II

- Serial Communication Interface – 8251
- Analog-to-Digital Converter Interfacing
- **Digital-to-Analog Converter Interfacing**
- Programmable Keyboard & Display Interface – 8279


Digital to Analog Converters

- Introduction & Types
- Specifications for DAC ICs
- DAC AD7523
- DAC 0800
- Interfacing
- Problems

DAC – Introduction


- Digital-to-Analog Converter (DAC) has the ability to convert digital signals to analog signals.
- DAC is a process in which digital words are applied to the input of the DAC and an analog output signal is generated to represent the respective digital input.
- In this conversion process, an 'N'-bit digital data can be mapped into a single analog output voltage.
- So, analog output of the DAC is a voltage that is some fraction of a reference voltage.
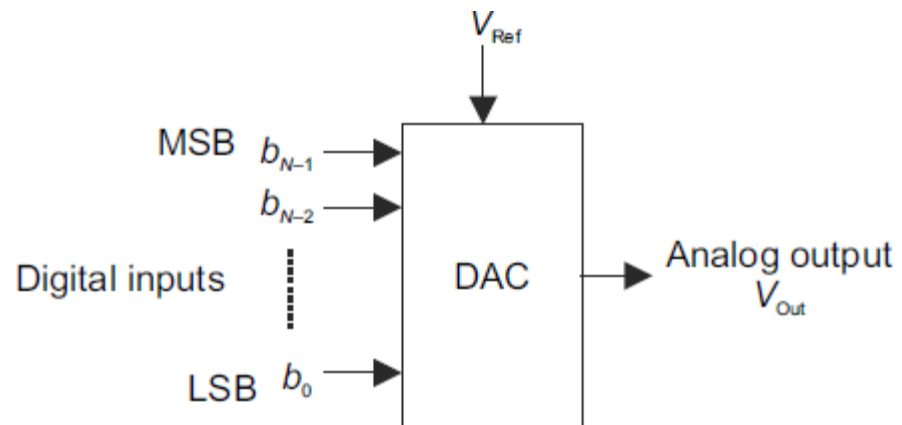
$$V_{\text{out}} = K \times V_{\text{Ref}}$$




DAC – Introduction

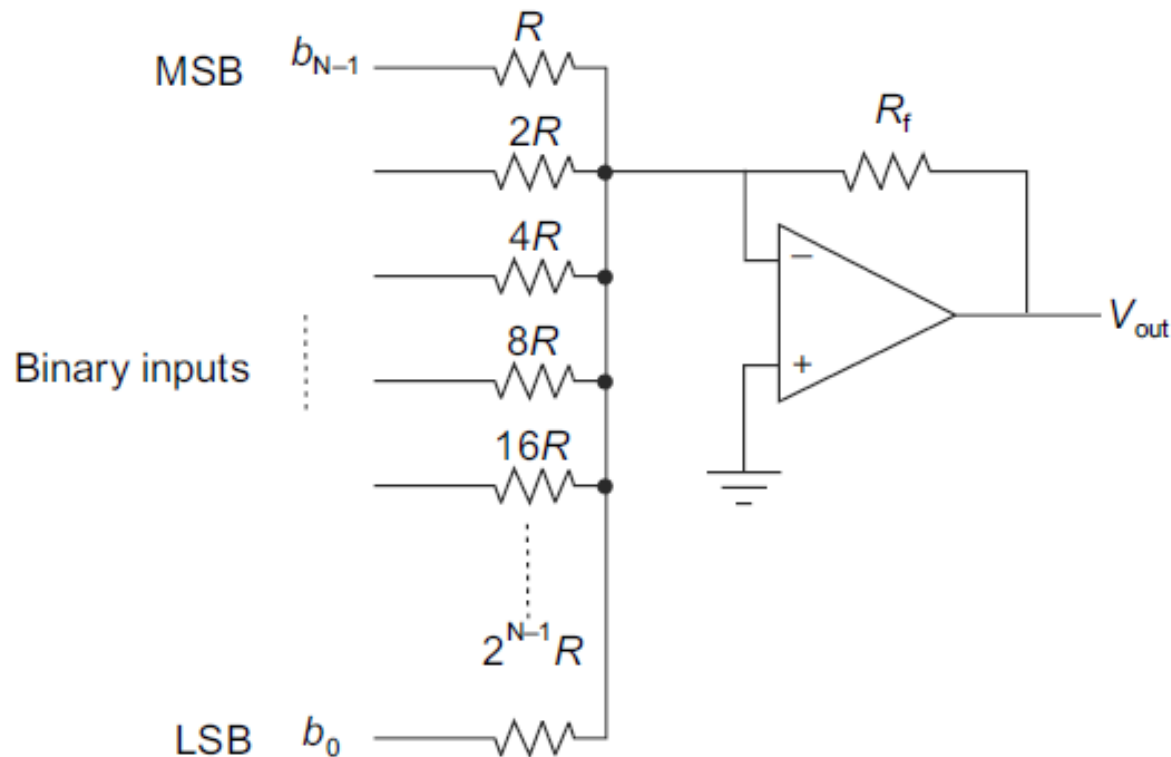- Classifications:
 - Weighted binary DAC
 - R-2R ladder
- N-bit Weighted binary DAC:



DAC – Introduction

- N-bit R-2R ladder DAC:

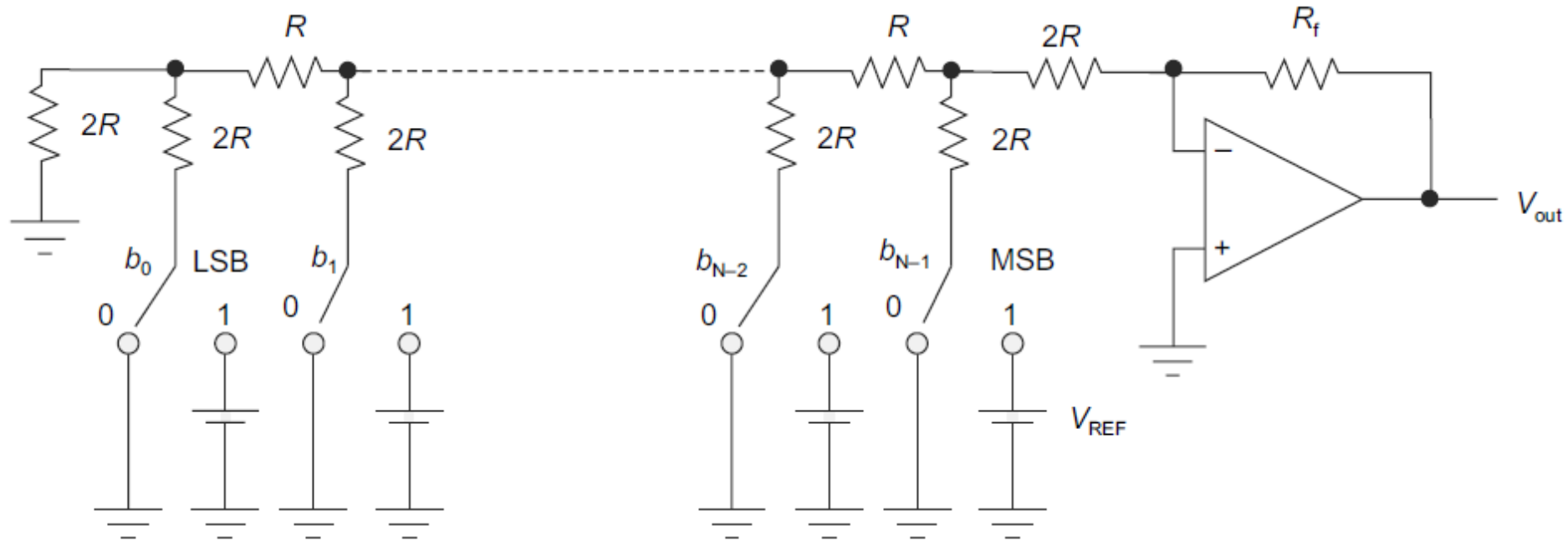

DAC – Specifications for DAC ICs

- **Resolution:**

$$\text{Resolution} = \frac{\text{Reference Voltage}}{\text{Number of Steps}} = \frac{V}{2^{N-1}}$$

- **Accuracy:**

- $\pm 0.25\%$

- **Offset/Zero Scale Error:**


- **Linearity:**

- **Temperature Sensitivity:**

- $\pm 50 \text{ ppm}/^\circ\text{C}$.


- **Settling Time:**

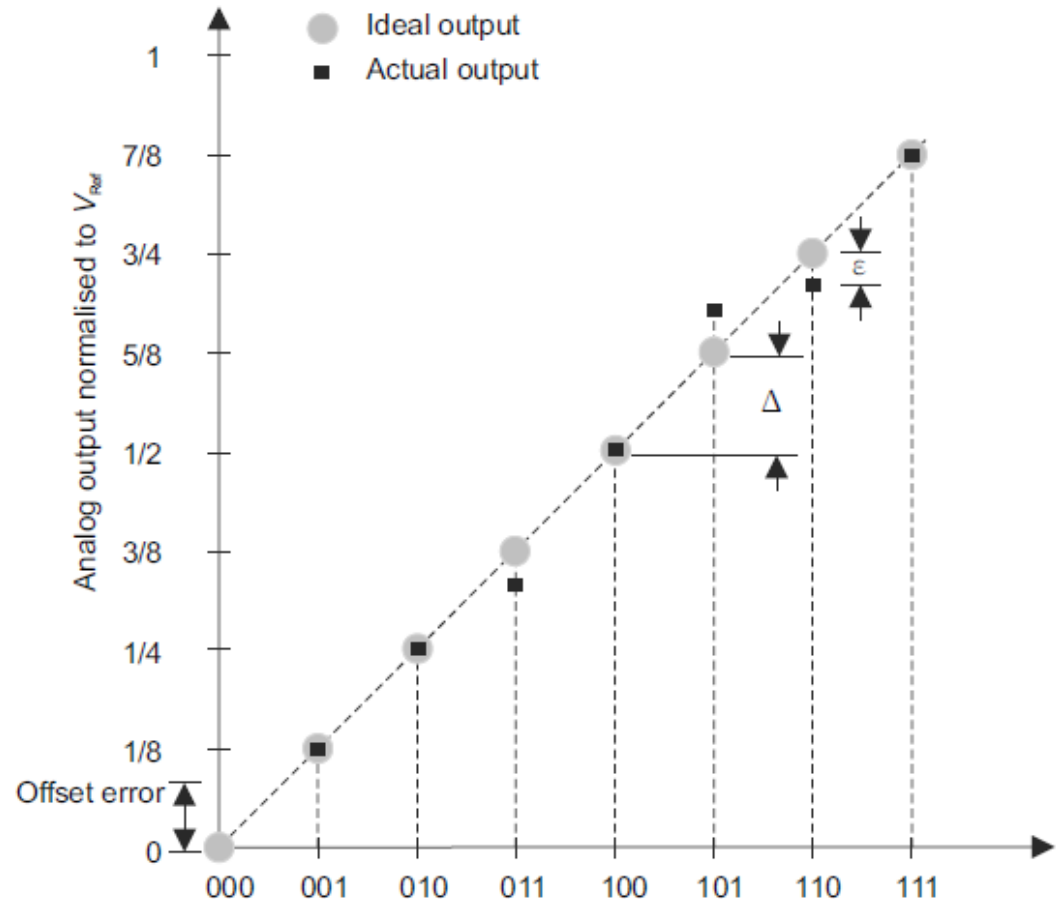- Time taken to settle within half LSB, 500ns



DAC AD 7523

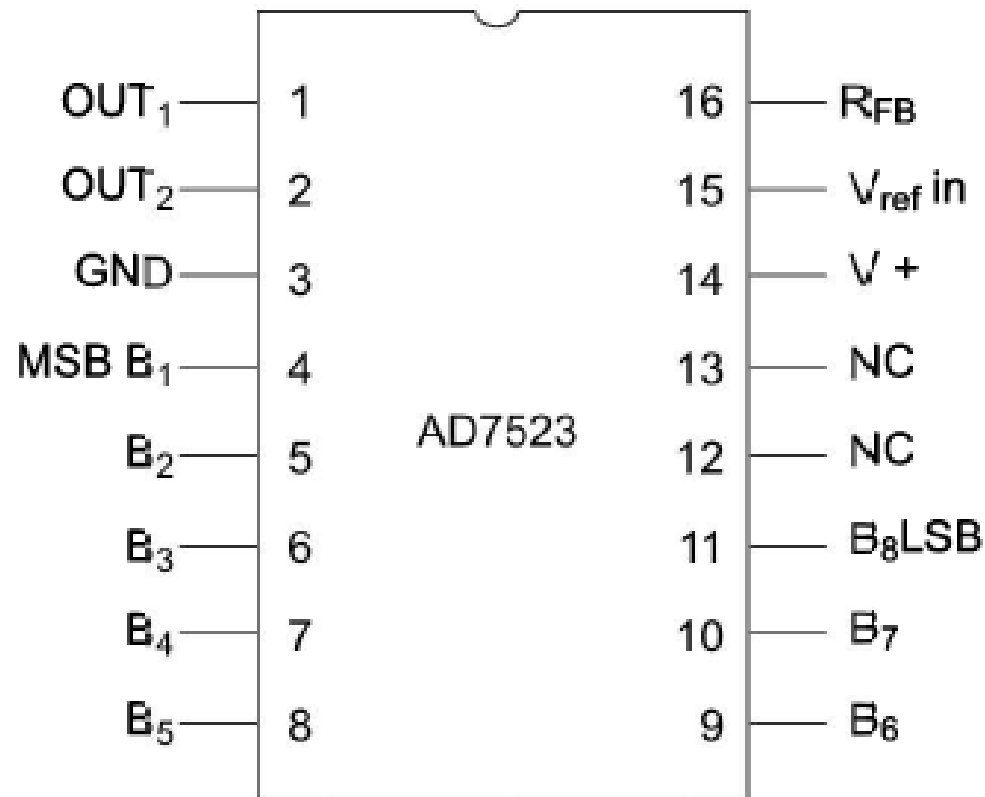
- R-2R ($R = 10k$)
- Supply range: 5V – 15V
- Max Analog output = +10V



DAC AD 7523

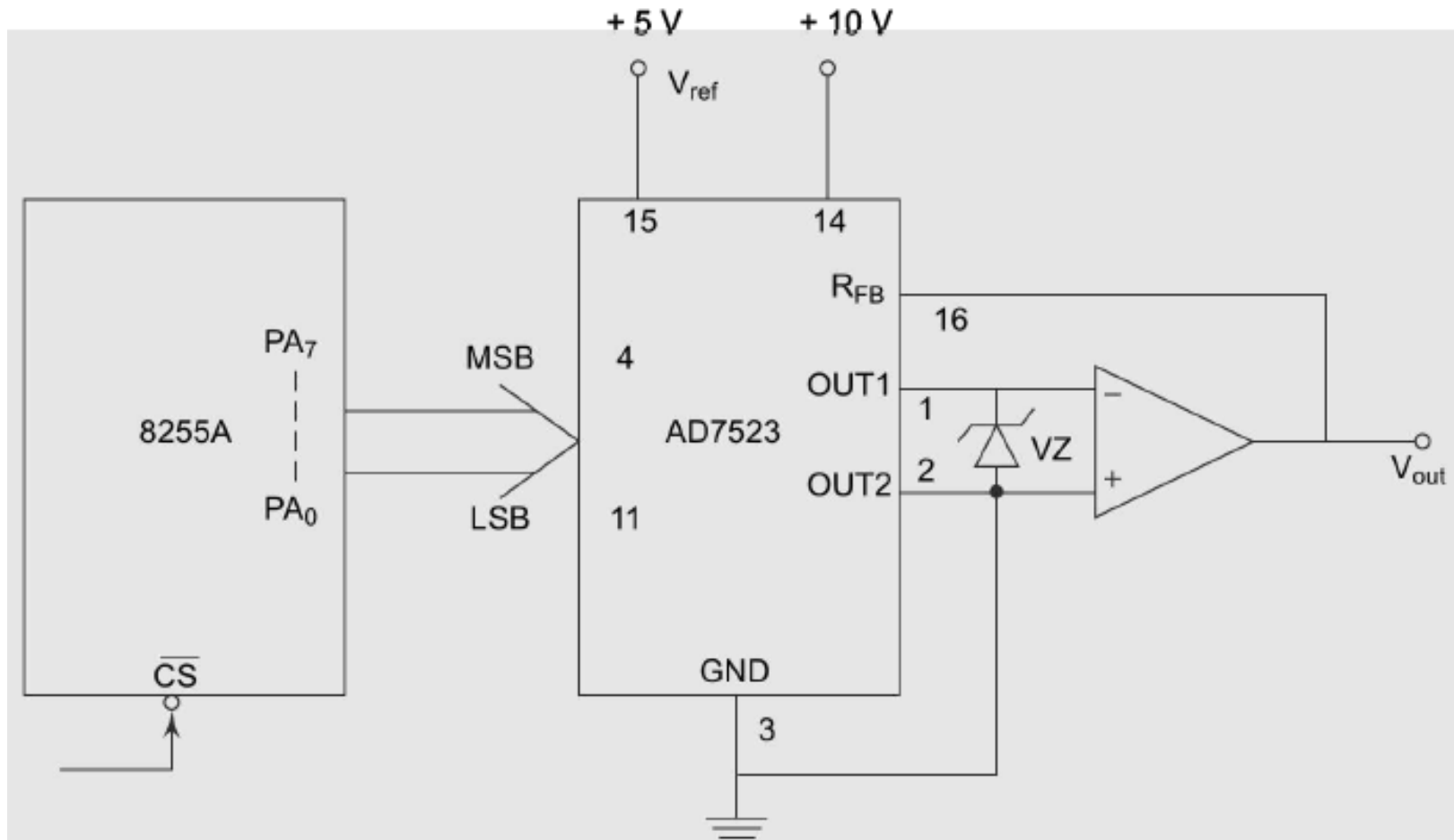Problem 1

Interface DAC AD7523 with an 8086 CPU running at 8 MHz and write an assembly language program to generate a sawtooth waveform of period 1 ms with V_{\max} 5V.




DAC AD 7523

ALP Program

```
ASSUME      CS : CODE
CODE        SEGMENT
START:      MOV AL,80 H          ; Initialise port A as output
            OUT CWR,AL          ; port
AGAIN:      MOV AL,00H          ; Start the ramp from 0V
BACK :      OUT PORTA,AL        ; Input 00H to DAC
            INC AL              ; Increment AL to increase ramp output
            CMP AL,0F2H         ; Is upper limit reached?
            JB BACK             ; If not, then increment the ramp
            JMP AGAIN           ; Else start again from 00H
CODE        ENDS
            END START
```

DAC 0800


- Settling time 100ms
- Operating range +4.5V to +18V

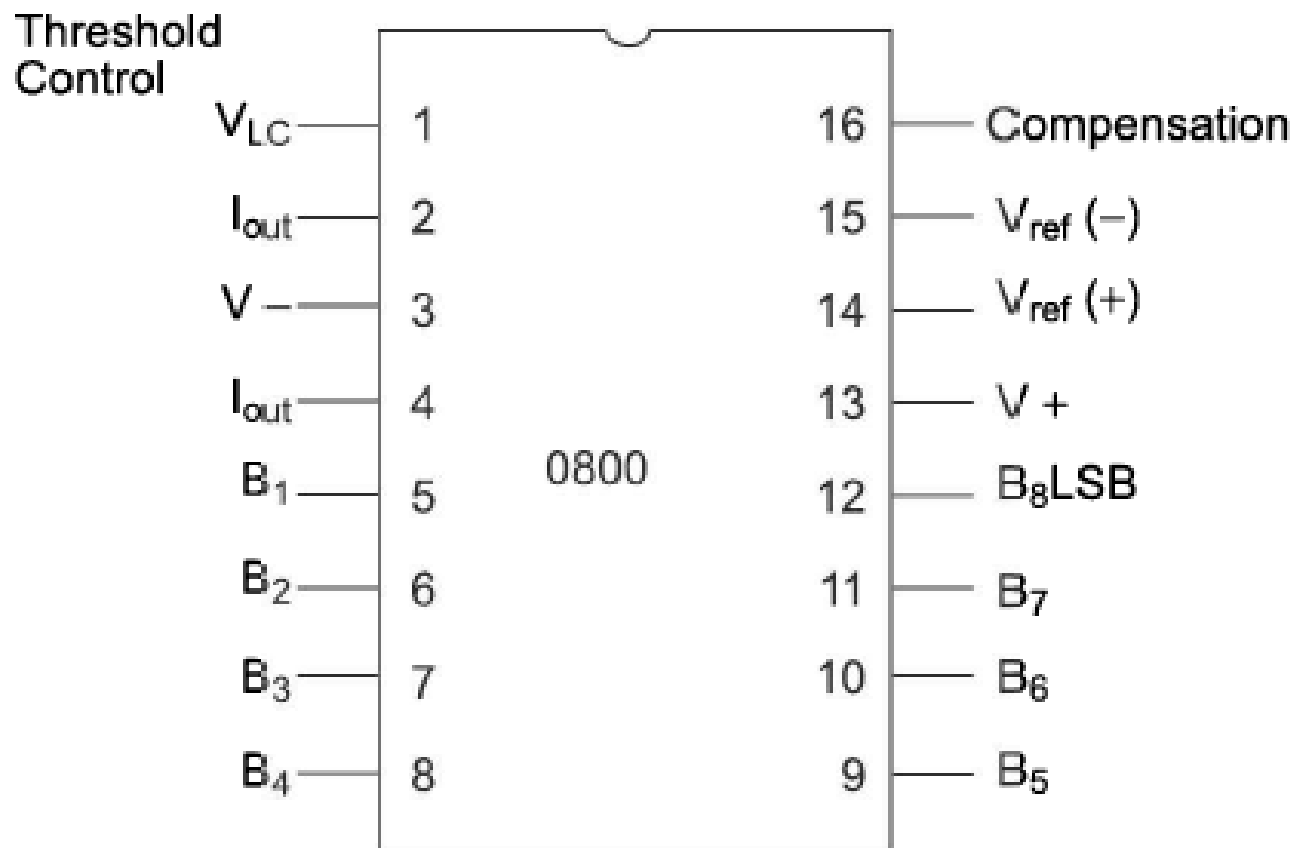

DAC 0800

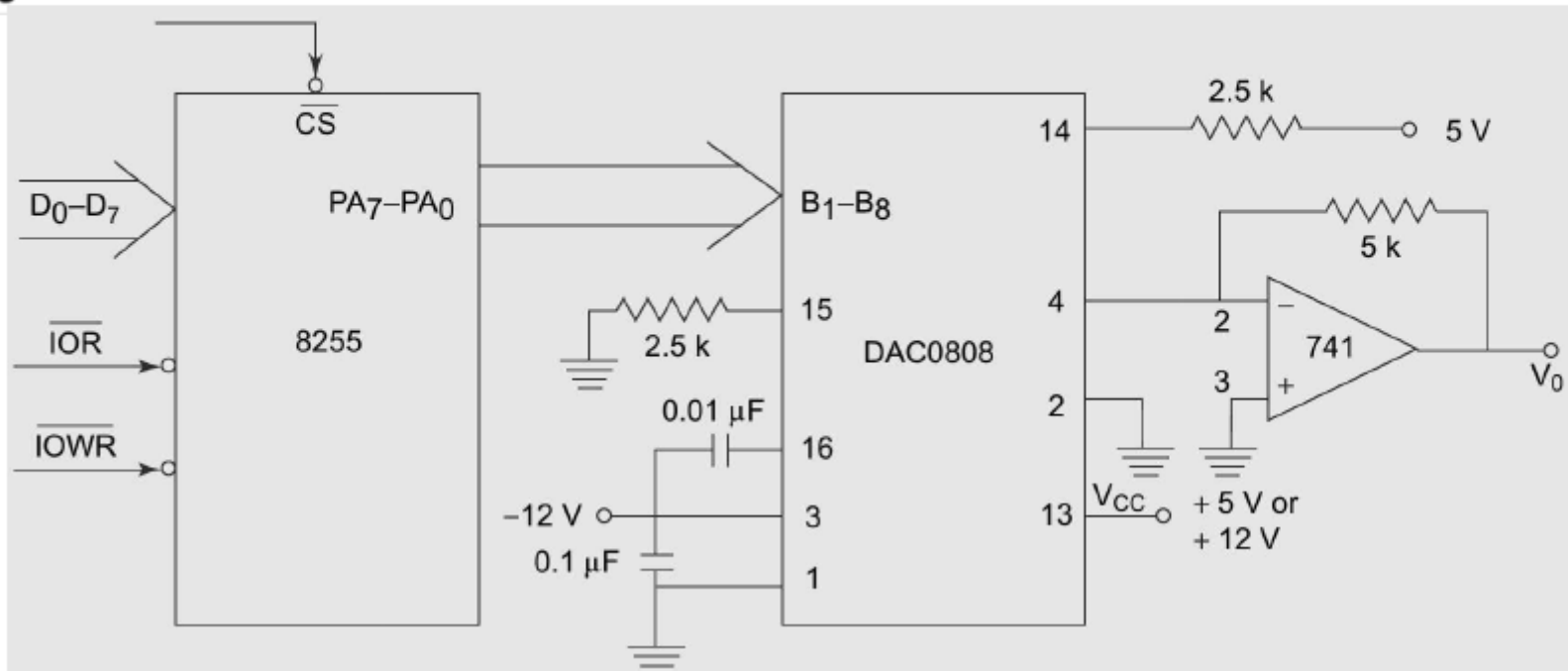Problem 2

Write an assembly language program to generate a triangular wave of frequency 500 Hz using the interfacing circuit given. The 8086 system operates at 8 MHz. The amplitude of the triangular wave should be +5 V.



The V_{ref+} should be tied to +5 V to generate a wave of +5V amplitude. The required frequency of the output is 500 Hz, i.e. the period is 2 ms. Assuming the wave to be generated is symmetric, the waveform will rise for 1 ms and fall for 1 ms. This will be repeated continuously. In the previous program, we have already written an instruction sequence for period 1 ms. Using the same instruction sequence one can derive this triangular waveform.

DAC 0800

ALP Program

```
ASSUME    CS : CODE
CODE      SEGMENT
START :   MOV AL,80 H           ; Initialise 8255 ports
          OUT CWR,AL           ; suitably.
          MOV AL,00H           ; Start rising ramp from
BACK :    OUT PORT A,AL        ; 0V by sending 00H to DAC.
          INC AL               ; Increment ramp till 5V
          CMP AL,FFH          ; i.e. FFH.
          JB BACK              ; If it is FFH then,
BACK1 :   OUT PORT A,AL        ; Output it and start the falling
          DEC AL               ; ramp by decrementing the
          CMP AL,00            ; counter till it reaches
          JA BACK1             ; zero. Then start again
          JMP BACK             ; for the next cycle.
CODE      ENDS
          END START
```